

What is Inrush Current?

When switching power supplies are first turned on, they present high initial currents as a result of filter capacitor impedance. These large filter capacitors act like a short circuit, producing an immediate inrush surge current with a fast rise time. The peak inrush current is several orders of magnitude greater than the circuit's steady state current. This power surge can seriously damage other components (such as welding switch contacts) or lead to blown fuses or tripped breakers.

Passive or Active Protection for Inrush Current?

There are several component options for inrush current limiting. The two most common alternatives are the use of NTC (Negative Temperature Coefficient) thermistors ([Surge Limiters](#)) or various forms of active circuits. However, the most appropriate inrush current suppression technique for a particular application depends on component pricing issues, the equipment's power level, and the frequency at which the equipment is likely to be exposed to inrush currents.

No single component solution can be best for every application. Each approach has its own advantages and disadvantages.

What is an Inrush Current Limiting Thermistor (Surge Limiter)?

NTC thermistors ([Surge Limiters](#)) are among the most common design options used in switching power supplies to prevent damage caused by inrush current surges. A thermistor is a thermally-sensitive resistor with a resistance that changes significantly and predictably as a result of temperature changes. The resistance of a Surge Limiting thermistor decreases as its temperature increases.

As the Surge Limiter self-heats, the current begins to flow through it. Its resistance begins to drop and a relatively small current flow charges the capacitors in the power supply. After the capacitors in the power supply become charged, the self heated Surge Limiter offers little resistance in the circuit. So low that the voltage drop is an insignificant factor with respect to the total voltage drop of the circuit.

What types of Inrush Current Limiting Thermistors ([Surge Limiters](#)) are available?

[Surge Limiters](#) are available in a wide range of initial resistance levels and current carrying capabilities. Ametherm produces [Surge Limiters](#) ranging from .2 to 220 ohms of initial resistance. Some designs are rated for less than one ampere while other are rated for up to 36 amperes.

Are NTC Thermistors Common for Inrush Current Protection?

A recent industry study, conducted by Data and Strategies Group, Inc., Framingham, MA, indicates that NTC thermistors are overwhelmingly the most popular type of device for inrush current suppression for power supplies. DSG's research indicates that NTC thermistors currently comprise more than 90% of the market for components for this purpose

What about the cool down time?

Because [Surge Limiters](#) heat after they suppress inrush currents, these devices require a cool-down time after power is removed. This cool-down or "recovery" time allows the resistance of the NTC thermistor to increase sufficiently to provide the required inrush current suppression the next time it is needed. An NTC's cool-down time varies according to the particular device, its mounting method and the ambient temperature. The typical cool-down time is roughly one minute.

What are other uses of NTC Thermistors

NTCs are used for many other applications as well. Besides their usefulness in inrush current suppression, NTC thermistors' accurate temperature response, high stability and excellent reliability are well-suited to many other areas of electronic design. For example, they are often used in applications such as temperature measurement,

temperature control, temperature compensation, voltage regulation, air-flow and liquid level sensing, and in creating time delay circuits.

NTC thermistors for Inrush Current Limiting

One advantage of NTC thermistors (Surge Limiters) over active circuits for inrush current suppression is lower component costs. Surge Limiters are typically less expensive than active circuit components. However, the exact cost of each component depends on the power level of the power supply for which it is intended. Typically, the higher the power level, the larger and more costly the component. The cost advantage of Surge Limiters over active circuits can be easily illustrated with the following example based on a 300W power supply. To provide inrush surge protection with Surge Limiters, the only components needed are two Surge Limiters, at a total cost of \$.80 or less for both thermistors.

A second Surge Limiter advantage is a simpler design. Because Surge Limiter-based surge suppression circuit designs typically involve fewer components, they are less complex than those involving active circuits. In turn, a simpler design reduces the time needed to design the inrush current suppression capability of the power supply. As a general rule of thumb, using Surge Limiters for inrush current suppression requires only about one-fifth the time needed to design a comparable active circuit.

Also, the Surge Limiter design provides greater manufacturing simplicity and lower reject rates. Fewer components means fewer assembly steps. A lower component count also decreases the potential for manufacturing rejects as a result of defective components.

Surge Limiter-based surge suppression designs typically require significantly less space on the power supply circuit board than active circuits. For applications where the space available is at a premium, this can be a critical consideration.

The failure mode when using an active circuit with a resistor usually requires component replacement. However, Surge Limiter-based in-rush surge suppression is self-protecting in the failure mode, because their resistance drops as temperature increases.

Active Circuits For Inrush Current

As mentioned previously, various types of "active" circuits are sometimes used as alternatives to NTC thermistors (Surge Limiters) for certain applications. These component alternatives include triacs, resistors, and thyristors.

An active circuit alternative is a triac (typically priced at about \$1.00 for a 300W power supply), plus a resistor (about \$.60), plus the circuit needed to drive the triac (\$.20 or more) for a total of \$1.80.

Despite the economic and design simplicity advantages Surge Limiters offer for inrush current suppression, there are some situations when an active circuit may provide a more appropriate solution. For example, active circuits can sometimes be a better choice than Surge Limiters when "hot restart" capabilities are critical. The advantage is related to the cool down/recovery time required for the resistance of the Surge Limiter to increase sufficiently to provide the required level of inrush current protection. If the power drops out for a period shorter than the specified recovery time, say, for a few seconds, the thermistor will not have an opportunity to cool down and return to its initial

level of resistance. When the power comes back on, the resistance is too low to provide sufficient inrush protection, so circuits could be damaged, fuses blown, etc.

Active circuits offer lower power dissipation than Surge Limiters at higher power ratings (typically those above 300W). Because these designs typically run much cooler than NTCs, their heat dissipation/heat sinking requirements are less.

Combination of NTC Thermistors and Active Circuits

There is a design technique engineers can employ to eliminate the problems posed by the cool-down/recovery time required for Surge Limiters to return to their initial level of resistance. Essentially, this involves designing inrush current protection to drop the Surge Limiters out of the circuit after they have performed their function. By removing them from the circuit once the initial surge has passed, the thermistors have an opportunity to cool down, so they are ready to respond to a subsequent surge after a power drop-out occurs.

This technique requires the addition of either a relay or a triac in parallel with the Surge Limiters, plus the circuits necessary to control it. All the components of the protection circuit would be in series with the input to the line. Once the inrush current has been absorbed by the thermistor, then either the triac starts firing or the relay closes. The simplest method of powering these components is from the power supply itself. Once the power supply starts, it closes the relay or fires the triac, dropping the thermistor out of the circuit and allowing it to cool down and regain its initial resistance, so it's ready to provide inrush current protection.

There are a lot of parameters which create the limits of switching lamp load. I try to explain:

The inrush current of both incandescent lamps and parallel compensated fluorescent lamps mainly depends on the impedance of your incoming power supply.

So we have a special test facility to create most worst case conditions known from the field.

With incandescent lamps:

- 707L at 10A has 200A inrush, 704L at 20A has 300A inrush. The inrush current is the limit, not the nominal lamp current.

(with resistive load the max. current is 20A for both 707L and 704L. The limit is getting the heat out of the relay, through the pcb pins.)

With fluorescent lamps, parallel compensated:

- 707L switching into 140 μ F creates 400A inrush, 704L at 200 μ F creates 600A inrush. Again the inrush current is the limit. The capacitance value is for easier calculation for the installer.

But if you exceed the capacitance value in some installations in the field you will exceed the inrush current.

Due to so many different electronic ballast loads we cannot define an exact nominal current, but you see that inrush is up to 100 times Inominal. (Not only 25 times).